
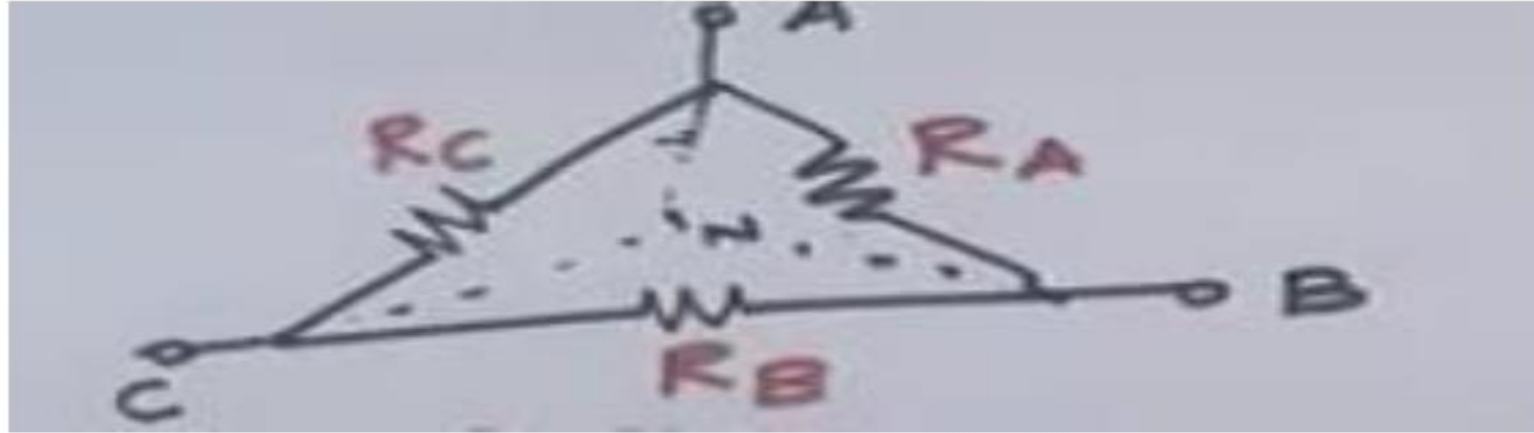


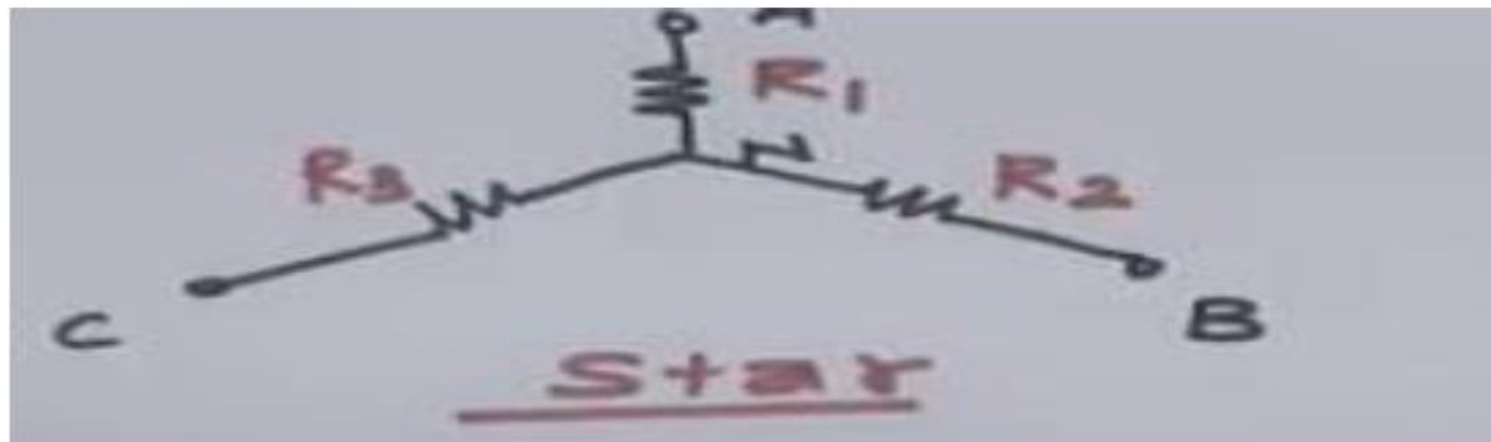
## Star Delta Transformation

In delta connection, three branches are connected nose to tail, they form a triangular closed loop, this configuration is referred as delta connection.



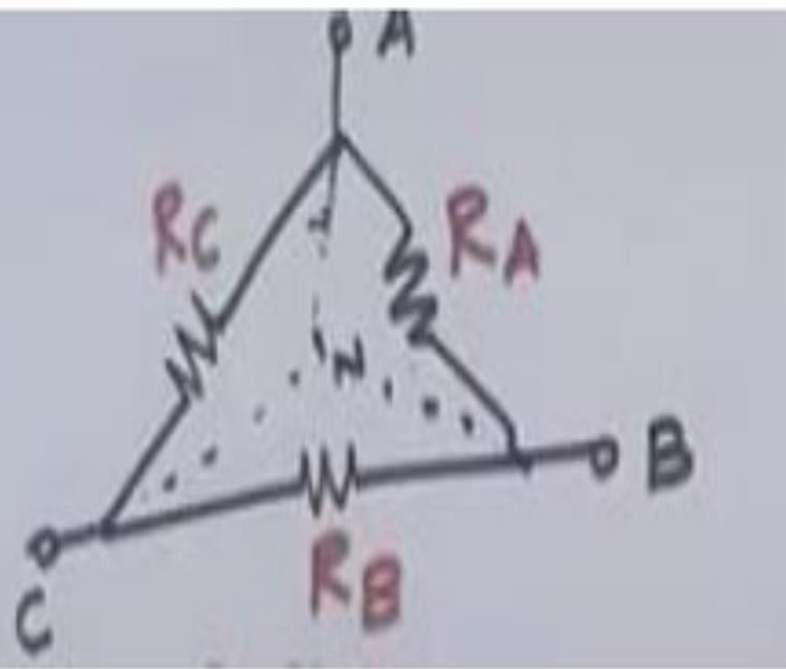When either terminal of three branches is connected to a common point to form a Y like pattern is known as **star connection**.





Eq. Resist. bet<sup>n</sup> A & B:

$$= R_A \parallel (R_B + R_C) = \frac{R_A(R_B + R_C)}{R_A + R_B + R_C} \text{--- ①}$$


similarly, Eq. Resist. bet<sup>n</sup> B & C:

$$= R_B \parallel (R_C + R_A) = \frac{R_B(R_C + R_A)}{R_B + R_C + R_A} \text{--- ②}$$

& Eq. Resist. bet<sup>n</sup> C & A:

$$= R_C \parallel (R_A + R_B) = \frac{R_C(R_A + R_B)}{R_C + R_A + R_B} \text{--- ③}$$

**Delta to star conversion**

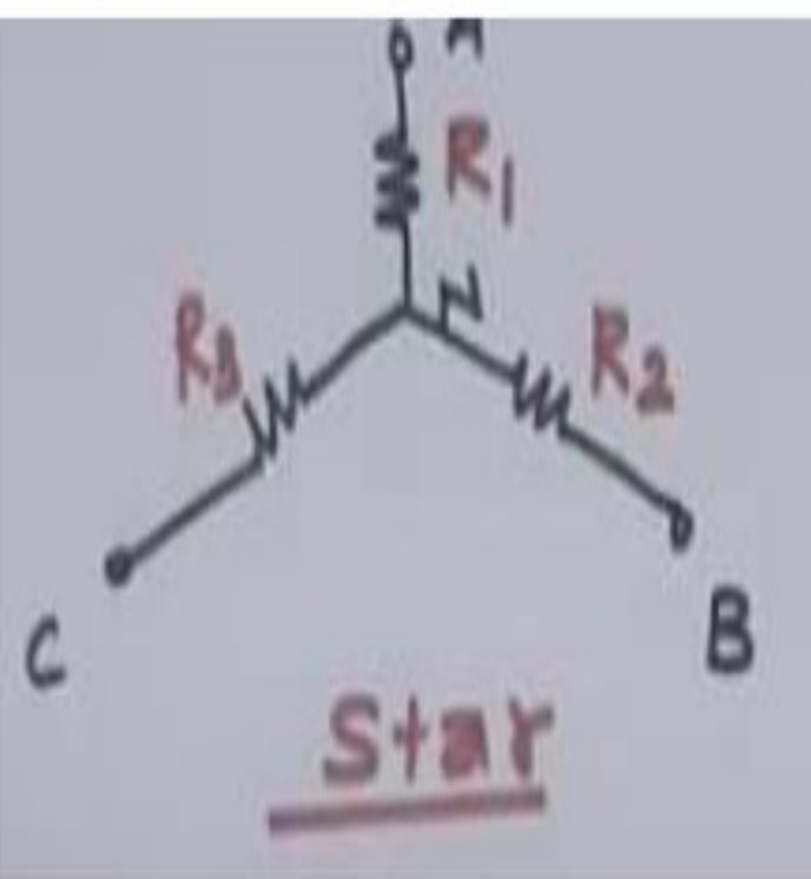

Eq. Resist. bet<sup>n</sup> A & B

$$R_1 + R_2 \text{ --- (4)}$$

Similarly,

B Eq. Resist. bet<sup>n</sup> B & C  
 $= R_2 + R_3 \text{ --- (5)}$

C Eq. Resist. bet<sup>n</sup> C & A  
 $= R_3 + R_1 \text{ --- (6)}$

Equating (1) & (4)

$$\frac{R_A(R_B + R_C)}{R_A + R_B + R_C} = R_1 + R_2 \text{ --- (7)}$$

Equating (2) & (5)

$$\frac{R_B(R_C + R_A)}{R_A + R_B + R_C} = R_2 + R_3 \text{ --- (8)}$$

Equating (3) & (6)

$$\frac{R_C(R_A + R_B)}{R_A + R_B + R_C} = R_3 + R_1 \text{ --- (9)}$$

Equation ⑦ - ⑧

$$\frac{R_A(R_B + R_C) - R_B(R_C + R_A)}{R_A + R_B + R_C} = R_1 - R_3 \text{ --- ⑩}$$

Adding Equ<sup>n</sup> ⑨ & ⑩

$$\frac{R_C \cdot R_A + \cancel{R_C R_B} + \cancel{R_A R_B} + R_A \cdot R_C - \cancel{R_B R_C} - \cancel{R_B R_A}}{R_A + R_B + R_C} = 2R_1$$

$$\frac{2 \cdot R_A R_C}{R_A + R_B + R_C} = 2R_1$$

$$R_1 = \frac{R_A \cdot R_C}{R_A + R_B + R_C}$$



Similarly,

$$R_2 = \frac{R_A \cdot R_B}{R_A + R_B + R_C}$$

&

$$R_3 = \frac{R_B \cdot R_C}{R_A + R_B + R_C}$$


Delta to Star

$$R_1 = \frac{R_{op} R_{cs}}{R_{ab} + R_{bc} + R_{ca}}$$

$$R_2 = \frac{R_{ab} R_{cs}}{R_{ab} + R_{bc} + R_{ca}}$$



$$R_3 = \frac{R_{ab} R_{bc}}{R_{ab} + R_{bc} + R_{ca}}$$
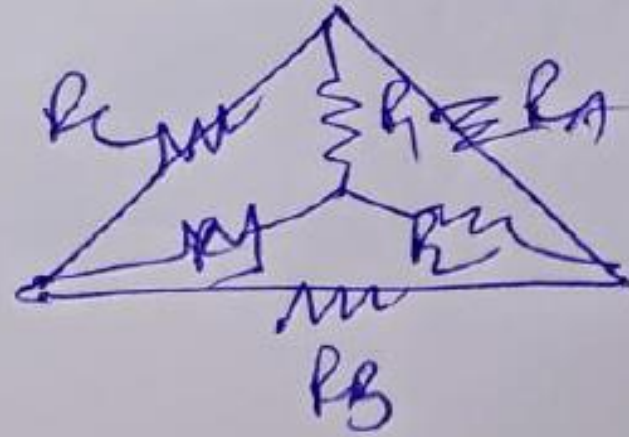
$$R_3 = \frac{R_{ab} \cdot R_{bc}}{R_{ab} + R_{bc} + R_{ca}}$$



# Star to delta

## Star to Delta Conversion

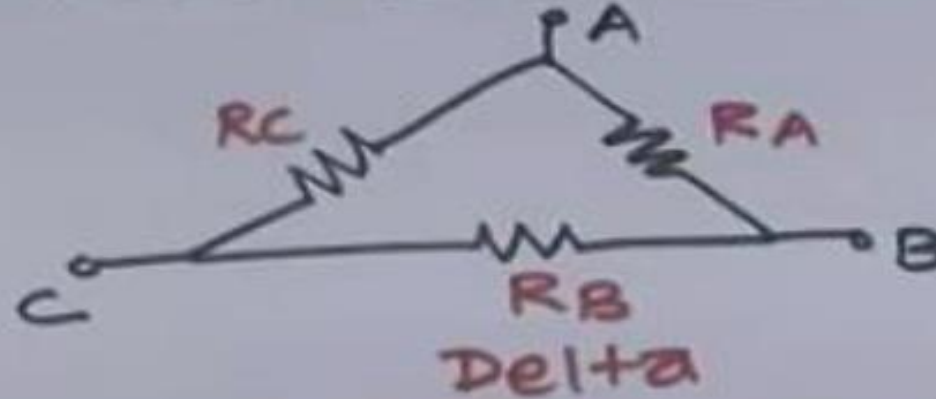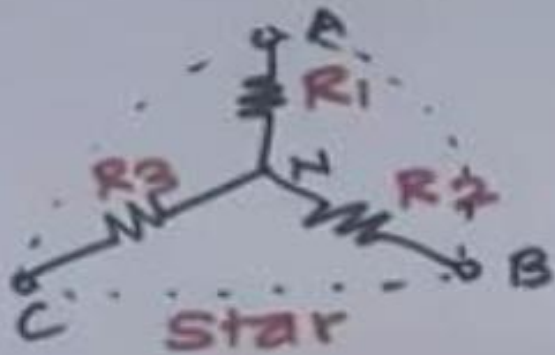

$$R_1 = \frac{R_A R_C}{R_A + R_B + R_C} ; R_2 = \frac{R_A R_B}{R_A + R_B + R_C} ; R_3 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$\begin{aligned} R_1 \cdot R_2 + R_2 \cdot R_3 + R_3 \cdot R_1 &= \frac{R_A^2 \cdot R_B \cdot R_C + R_A \cdot R_B^2 \cdot R_C + R_A R_B R_C}{(R_A + R_B + R_C)^2} \\ &= \frac{R_A R_B R_C (R_A + R_B + R_C)}{(R_A + R_B + R_C)^2} \end{aligned}$$



$$R_1 = \frac{R_A R_C}{R_A + R_B + R_C} ; R_2 = \frac{R_A R_B}{R_A + R_B + R_C} ; R_3 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_A^2 R_B R_C + R_A R_B^2 R_C + R_A R_B R_C^2}{(R_A + R_B + R_C)^2}$$

$$= \frac{R_A R_B R_C (R_A + R_B + R_C)}{(R_A + R_B + R_C)^2}$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_A R_B R_C}{R_A + R_B + R_C}$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = R_A \cdot R_3$$

$$\frac{R_1 R_2}{R_3} + R_2 + R_1 = R_A$$



$$R_1 R_2 + R_2 R_3 + R_3 R_1 = R_A \cdot R_3$$

$$\boxed{\frac{R_1 R_2}{R_3} + R_2 + R_1 = R_A}$$

$$\boxed{R_2 + R_3 + \frac{R_2 R_3}{R_1} = R_B}$$

$$R_1 + R_3 + \frac{R_1 R_3}{R_2} = R_C$$

# Star to Delta Conversion

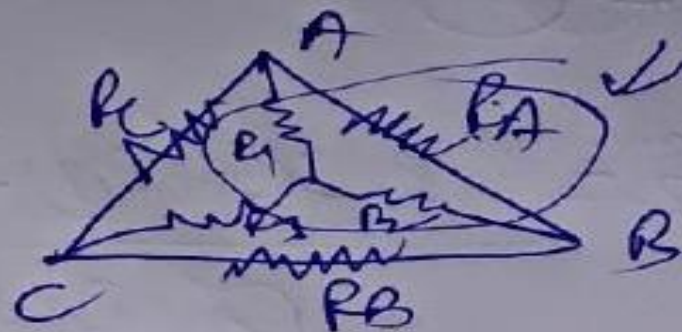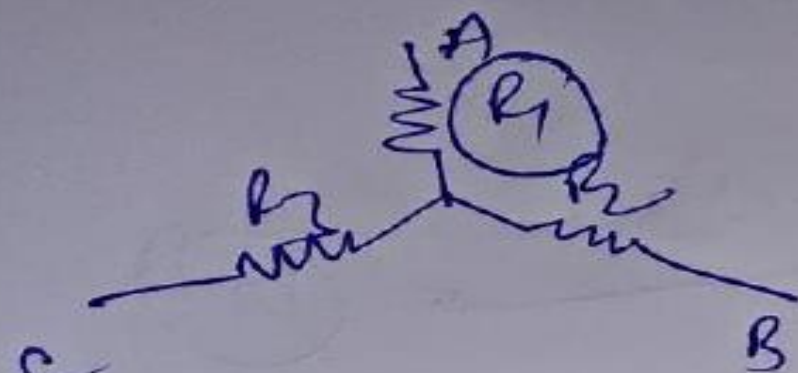

$$R_A = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

[ Sum of front resistor +  
multi of front res  
 $R_1$  ]

$$R_B = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_C = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$